



Computer Architecture HW2: Arithmetic Logic Unit (ALU)

TA: Yung-Chin Chen (陳永縉)

Email: b08901061@ntu.edu.tw

Due Monday, 11/20, 23:59



Data Preparation

◆ Decompress HW2.zip

- ◆ \$ unzip HW2.zip

◆ Direction hierarchy:

◆ 00_TB

- HW2_tb.v → testbench file
- Pattern → test pattern
 - I0
 - I1
 - ...

◆ 01_RTL

- 00_license.f → EDA tool license source command
- 01_run.f → vcs/ncverilog command
- 99_clean_up.f → Command to clean temporary data
- HW2.v → Your design



Goal


- ◆ To implement common arithmetic operations
 - ◆ Signed: **ADD**, **SUB**, **SLT**, **SRA**
 - ◆ Unsigned: **AND**, **OR**
 - ◆ Multicycle unsigned **MUL** and **DIV**
- ◆ Combine the 8 operations above into a single unit (ALU)

- ◆ In this homework, you will learn:
 - ◆ How to use assignments with **wire**
 - ◆ How to use always blocks with **reg**
 - ◆ How to implement combinational and sequential circuits
 - ◆ How to design finite state machines for state control
 - ◆ How to develop a good verilog coding style



Quick Review: Multiplication Circuit

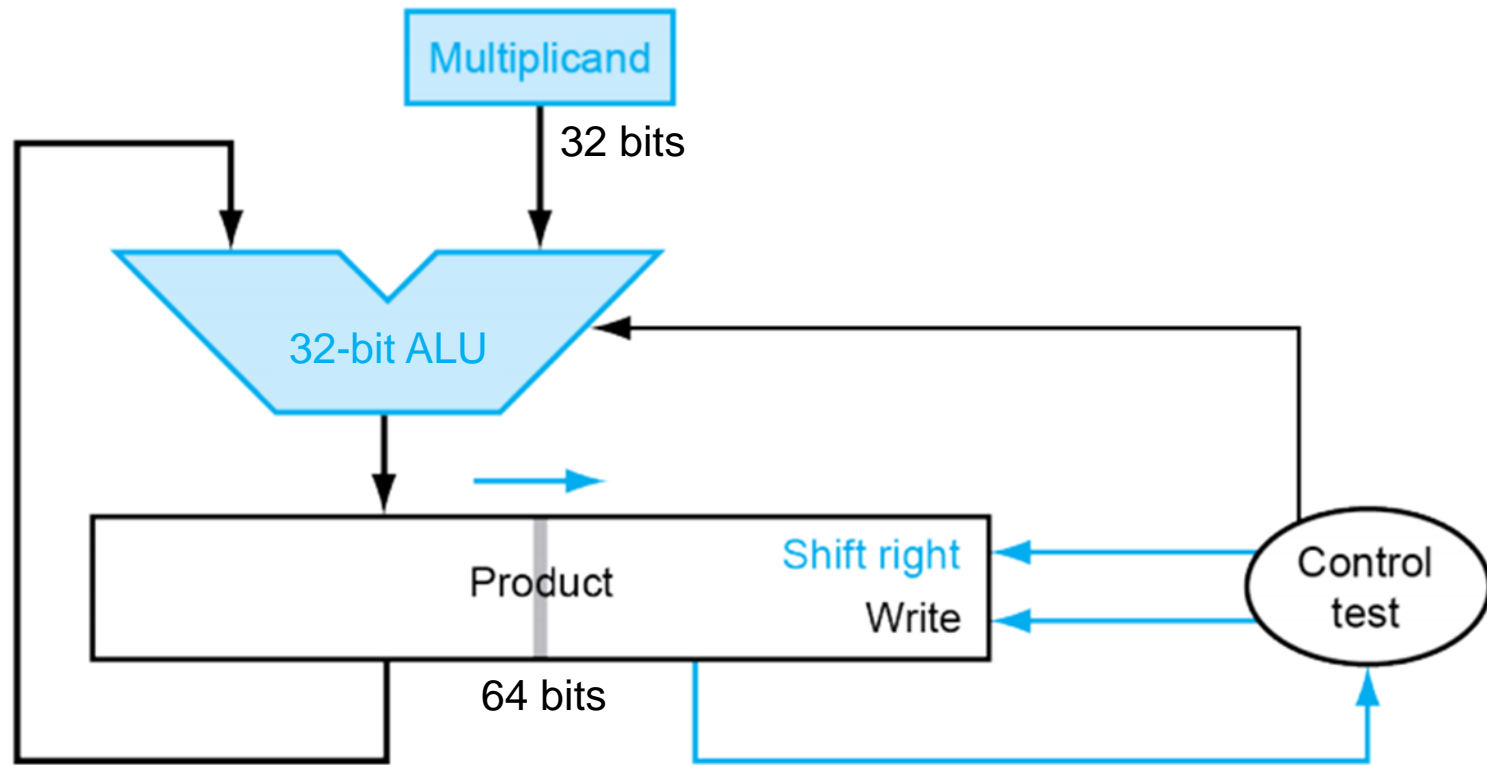
- ◆ Reduced register consumption
- ◆ Reduced size of ALU





Quick Review: Division Circuit

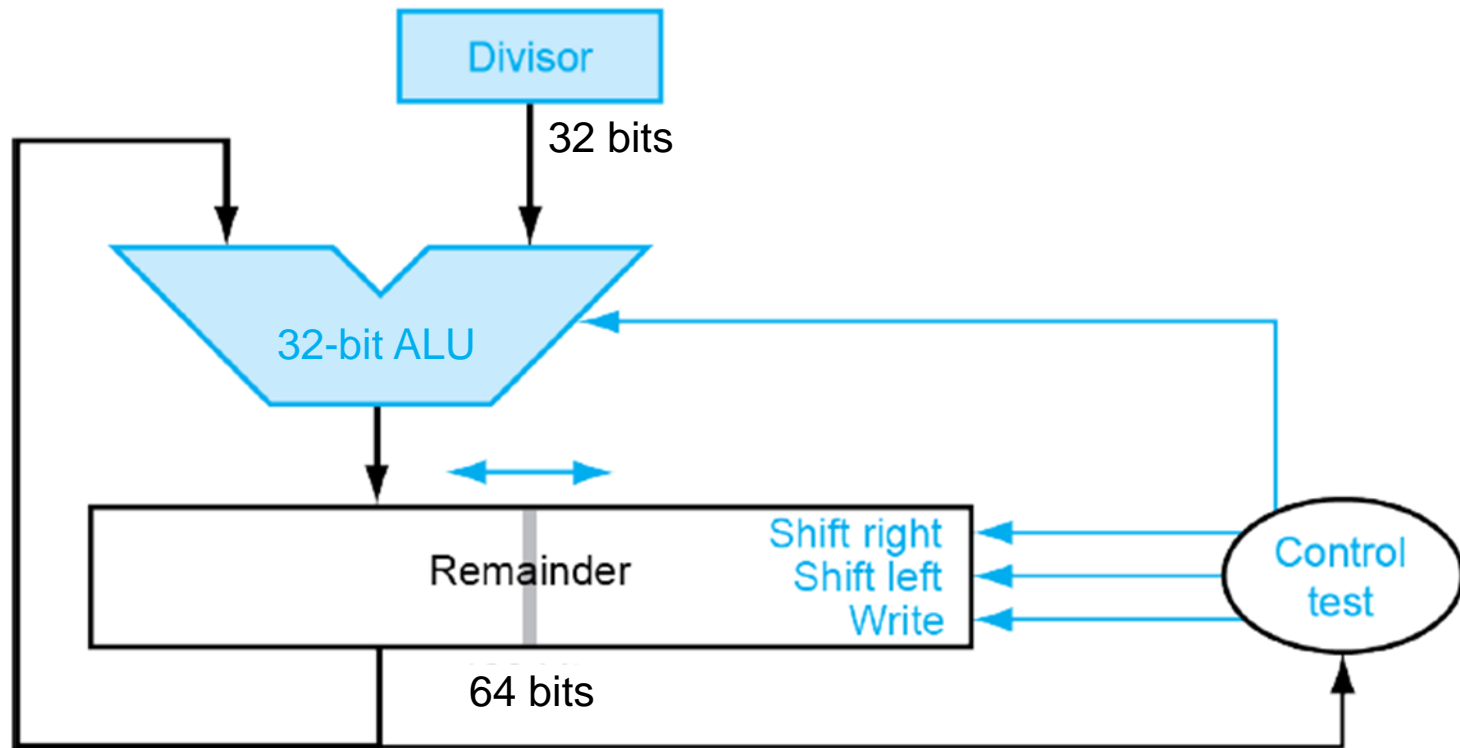
- ◆ Reduced register consumption
- ◆ Reduced size of ALU






Observation

 - ◆ The structures of both multiplier and divider are similar
 - ◆ Operand register
 - ◆ Shift register
 - ◆ ALU
- ◆ Reuse the hardware!





Block Diagram

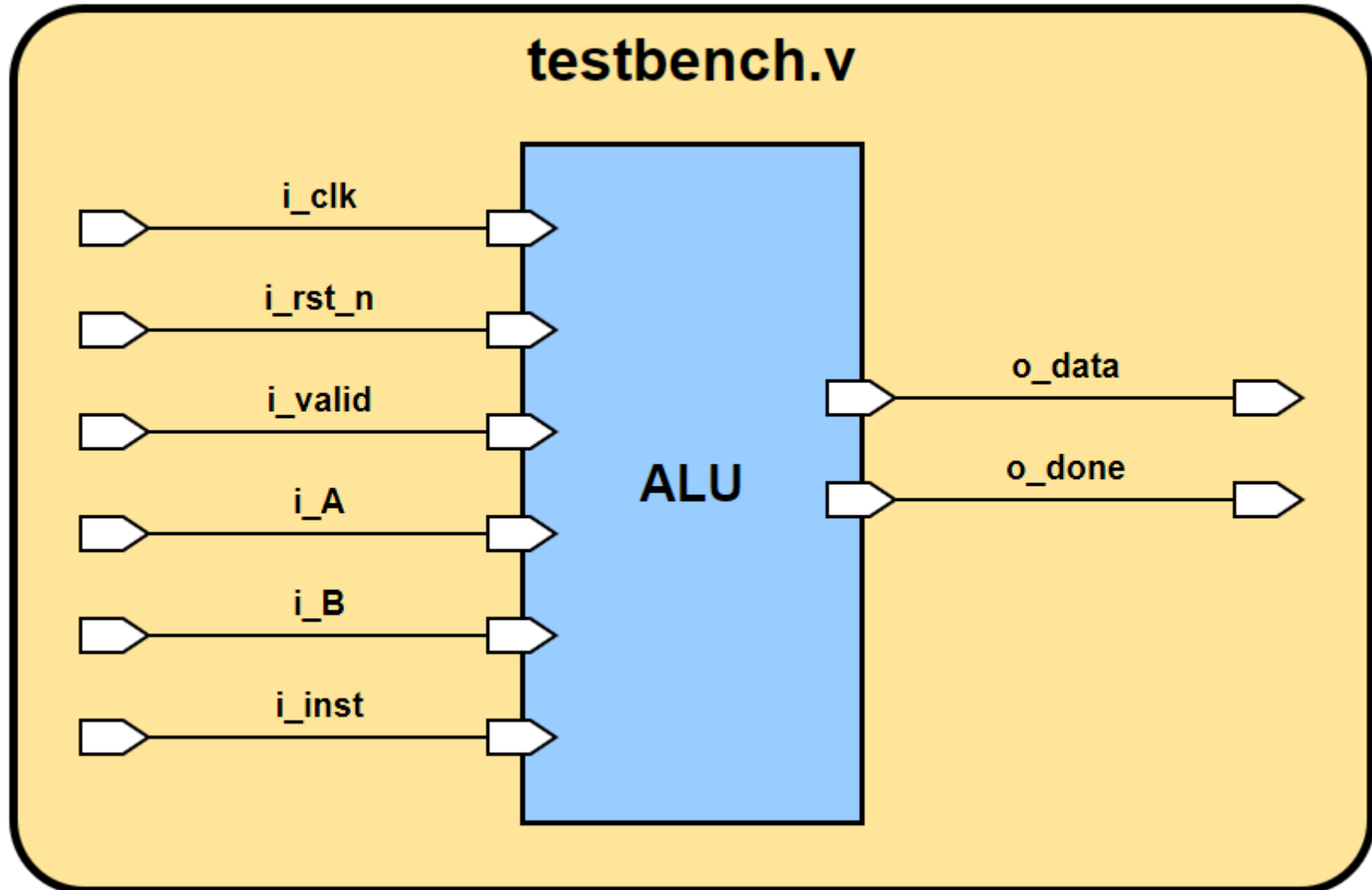



Specification – I/O

Signal Name	I/O	Width	Description
i_clk	I	1	Clock signal
i_rst_n	I	1	Active low asynchronous reset
i_valid	I	1	Valid input data when valid = 1
i_A	I	32	32-bit input data A
i_B	I	32	32-bit input data B
i_inst	I	3	Operation instruction
o_data	O	64	64-bit output data
o_done	O	1	Set high with valid output data



Specification – I/O (cont.)

- ◆ Do not Modify the I/O parts !!!

```
module ALU #(
    parameter DATA_W = 32
)
(
    input                i_clk,
    input                i_rst_n,

    input                i_valid,
    input [DATA_W - 1 : 0] i_A,
    input [DATA_W - 1 : 0] i_B,
    input [                2 : 0] i_inst,

    output [2*DATA_W - 1 : 0] o_data,
    output                o_done
);
// Do not Modify the above part !!!
```



Specification – Other Description

- ◆ All inputs are synchronously fed within negative edge clock.
- ◆ All outputs should be synchronized at clock rising edge.
- ◆ All outputs should be reset when i_rst_n is **low**. Active low asynchronous reset is used only once.
- ◆ Instructions are given by i_inst when i_valid is **high**.
- ◆ i_valid stays high for only 1 cycle.
- ◆ The runtime of the design should be within 10000 cycles
- ◆ **The operators “ * ” and “ / ” are forbidden**



Design Description

- ◆ The followings are the operation modes you need to design for this homework:

Operations	i_inst	Meaning	Note
ADD	3'd0	$A + B$	Signed operation
SUB	3'd1	$A - B$	Signed operation
AND	3'd2	$A \& B$	unsigned operation
OR	3'd3	$A B$	unsigned operation
SLT	3'd4	If $A < B$ then output 1; else output 0.	signed operation
SRA	3'd5	Shift A with B bits right	signed operation
MUL	3'd6	Multicycle $A * B$	unsigned operation
DIV	3'd7	Multicycle A / B	unsigned operation



Design Description (cont.)

◆ Overflow issue for **ADD, SUB**

- ◆ Set o_data =
$$\begin{cases} 2^{31} - 1, & \text{if the result} > 2^{31} - 1 \\ -2^{31}, & \text{if the result} < -2^{31} \end{cases}$$

◆ **MUL** and **DIV** operation

◆ Multiplication

- Unsigned input (32b)
- out = i_A × i_B (32b × 32b → 64b)

◆ Division

- Unsigned input (32b)
- quotient = i_A / i_B (quotient is 32b)
- remainder = i_A % i_B (remainder is 32b)
- out = {remainder, quotient}



Design Issues

- ◆ **Require 1 cycle to load data**
- ◆ **Require 32 cycles to do MUL/DIV**
- ◆ **Require 1 cycle to do the rest operations**
- ◆ **Require 1 cycle to output data**

- ◆ **Consider CPU is issuing a task to ALU**
 - ◆ Valid input to ALU for only 1 cycle
 - ◆ Expect to receive ready output from multiplication/division after 32 cycles
 - ◆ Expect to receive ready output from operations after 1 cycle



Load Data

- ◆ Already implemented “Load Data” for you
- ◆ Please directly use the loaded data for computation


```
// load input
always @(*) begin
    if (i_valid) begin
        operand_a_nxt = i_A;
        operand_b_nxt = i_B;
        inst_nxt      = i_inst;
    end
    else begin
        operand_a_nxt = operand_a;
        operand_b_nxt = operand_b;
        inst_nxt      = inst;
    end
end
```

```
// Todo: Sequential always block
always @(posedge i_clk or negedge i_rst_n) begin
    if (!i_rst_n) begin
        state      <= S_IDLE;
        operand_a  <= 0;
        operand_b  <= 0;
        inst       <= 0;
    end
    else begin
        state      <= state_nxt;
        operand_a  <= operand_a_nxt;
        operand_b  <= operand_b_nxt;
        inst       <= inst_nxt;
    end
end
```



Waveform

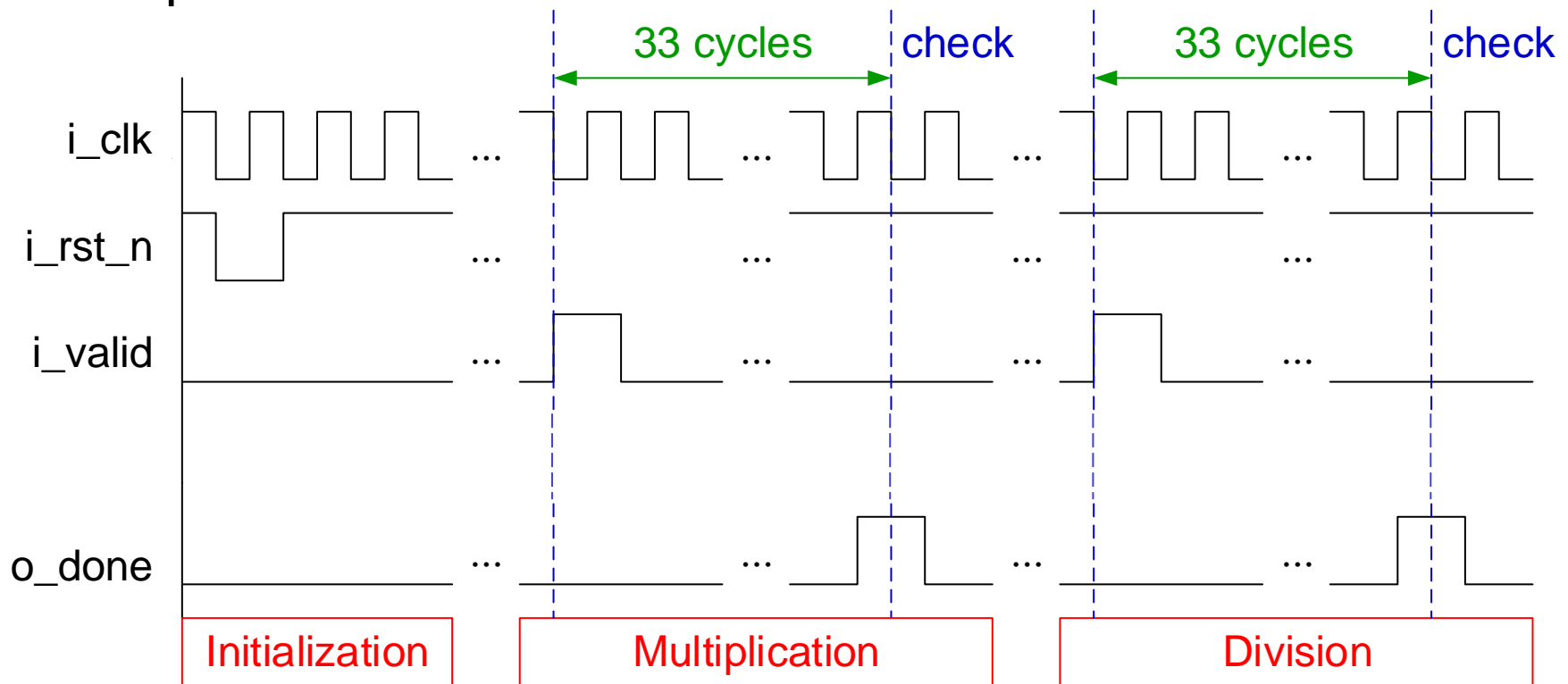
- ◆ The testbench checks the result at the negedge of clock if o_done is **high**
- ◆ The testbench checks if the cycles used by each operation is correct





Finite State Machine (FSM)

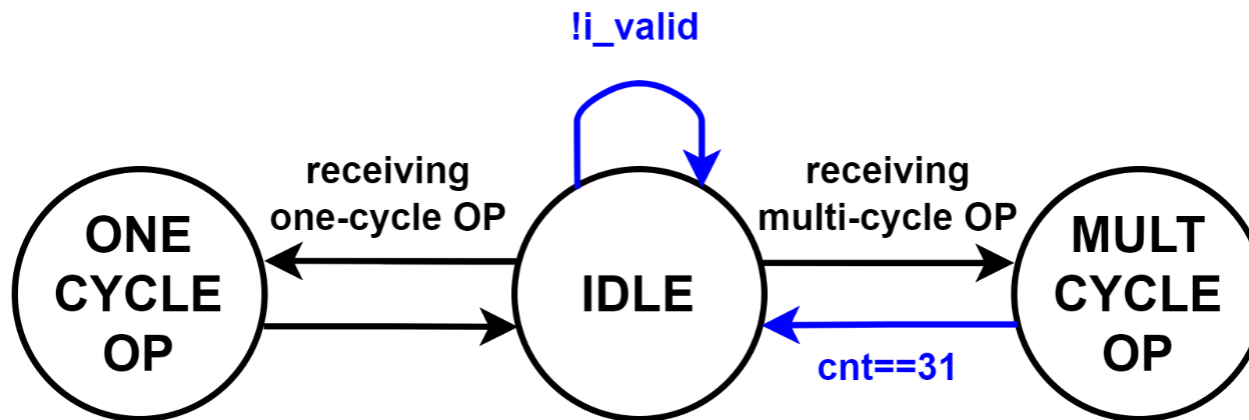
- ◆ Categorizing operation modes based on operation cycles





Finite State Machine (FSM)

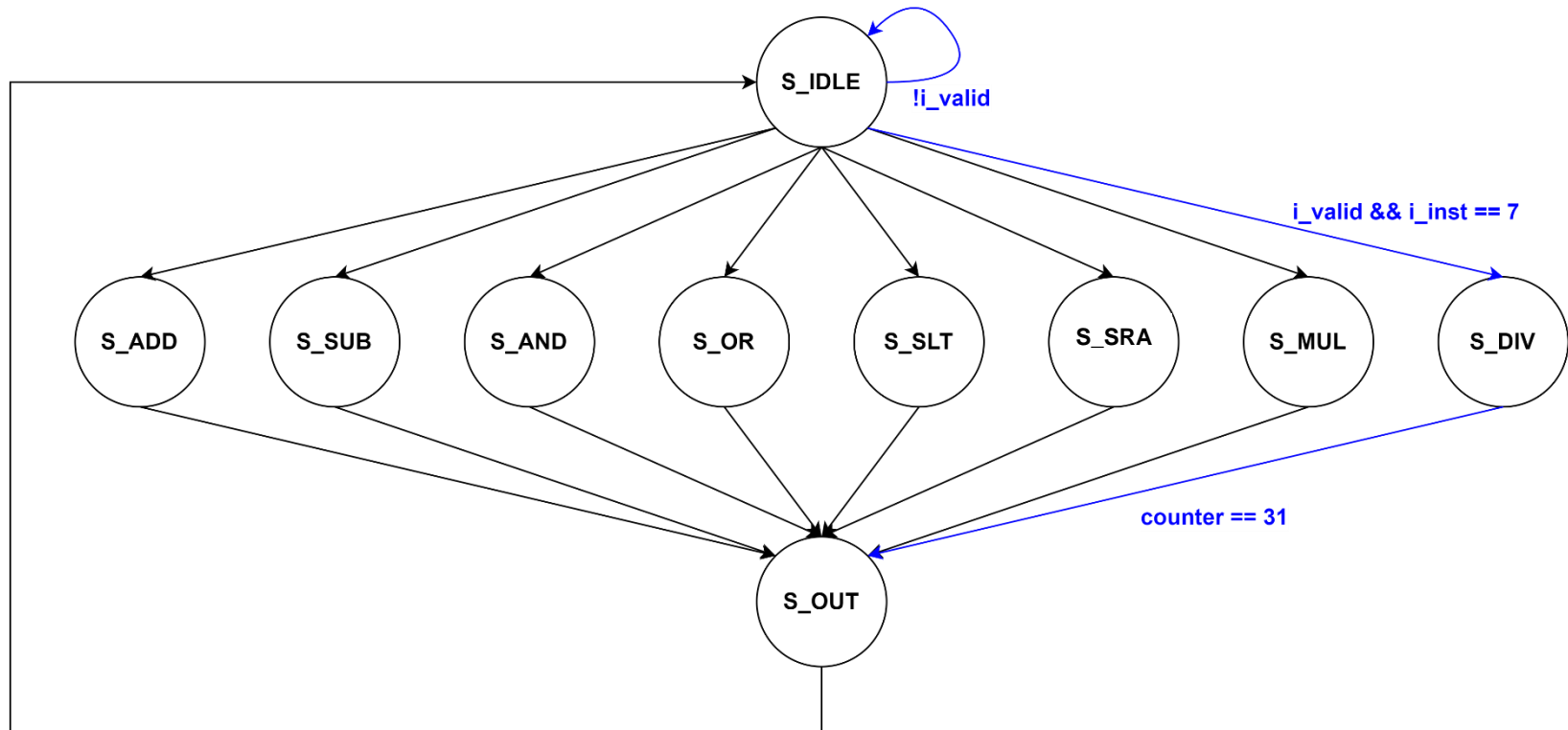- ◆ Independent state for each operation mode



- ◆ You can design your own FSM



Todo: FSM

◆ Define your finite state machine

```
// 1. FSM based on operation cycles
parameter S_IDLE      = 4'd0;
parameter S_ONE_CYCLE_OP = 4'd1;
parameter S_MULTI_CYCLE_OP = 4'd2;
```

```
// 2. FSM based on operation modes
// parameter S_IDLE = 4'd0;
// parameter S_ADD  = 4'd1;
// parameter S_SUB  = 4'd2;
// parameter S_AND  = 4'd3;
// parameter S_OR   = 4'd4;
// parameter S_SLT  = 4'd5;
// parameter S_SRA  = 4'd6;
// parameter S_MUL  = 4'd7;
// parameter S_DIV  = 4'd8;
// parameter S_OUT  = 4'd9;
```

◆ Sequential and Combinational Blocks

```
// Todo: Sequential always block
always @(posedge i_clk or negedge i_rst_n) begin
    if (!i_rst_n) begin
        state <= S_IDLE;
    end
    else begin
        state <= next_state;
    end
end
```

```
// Todo: FSM
always @(*) begin
    case(state)
        S_IDLE      :
        S_ONE_CYCLE_OP :
        S_MULTI_CYCLE_OP :
        default : state_nxt = state;
    endcase
end
```



Todo: Counter


◆ Hint

- ◆ Counter counts from 0 to 31 when the state is MUL or DIV
- ◆ Otherwise, keep it zero



Todo: ALU output


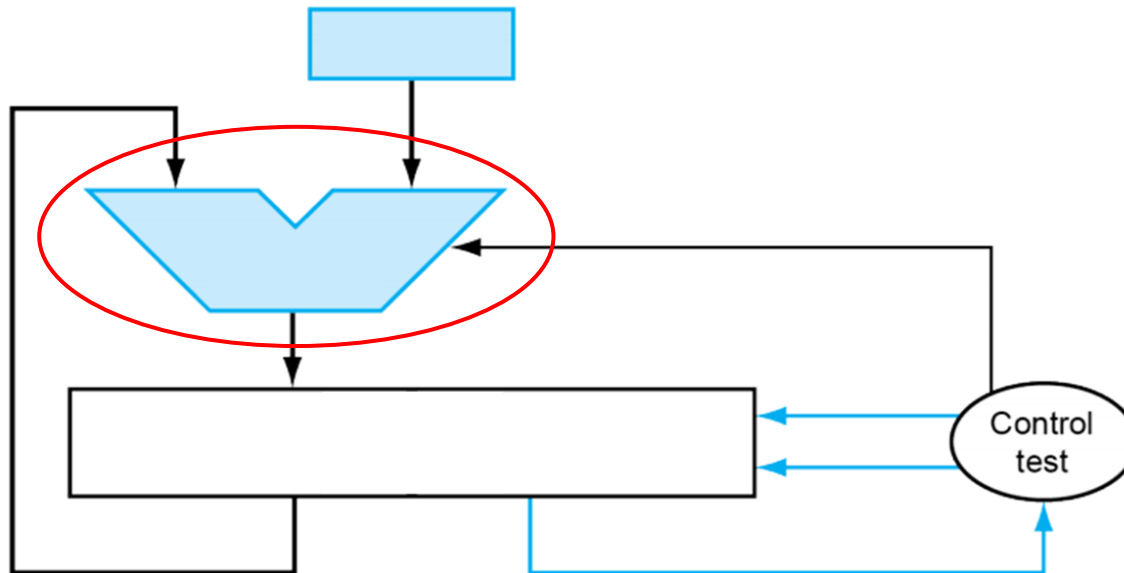
- ◆ Multiplication: addition / Division: subtraction
- ◆ Other operations
- ◆ You should consider
 - ◆ Bit width of ALU (to handle overflow)
 - ◆ Which bit range of shift register should be transmitted to ALU
 - ◆ The operation in ALU given current state





Todo: Shift Register

 
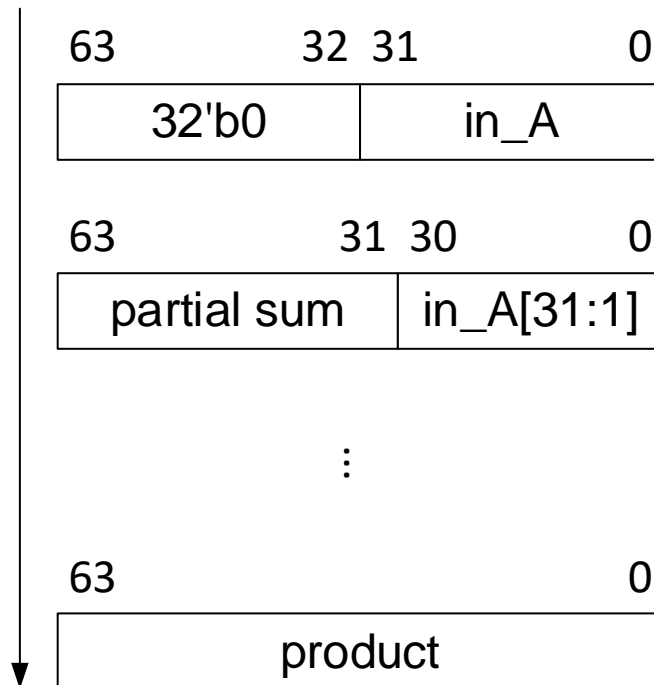
- ◆ Load data to the low 32 bits when the state is IDLE and valid = 1
- ◆ Multiplication: update data and **right shift**
- ◆ Division: update data and **left shift**





Todo: Shift Register (Cont.)

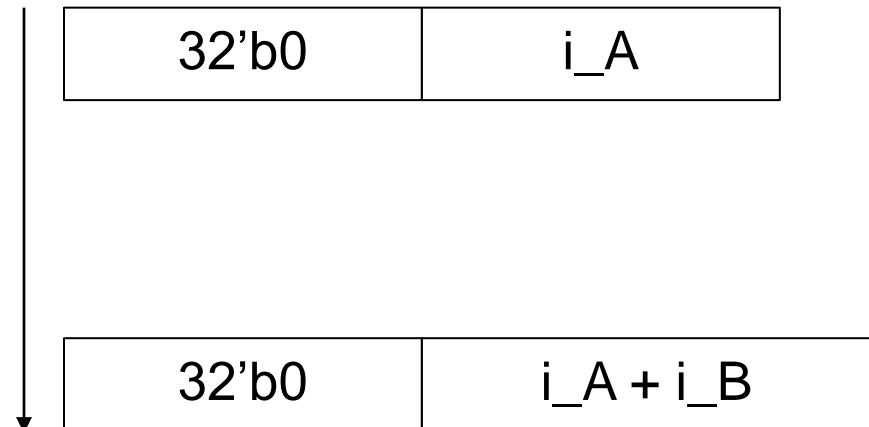 - ◆ Load data to the low 32 bits when the state is IDLE and $\text{valid} = 1$
- ◆ Other operations: (ex.)
 - ◆ AND: update data
 - ◆ ADD: update data





Todo: Output Control

- ◆ Relate output port “out” to shift register
- ◆ When is your circuit “ready” to output?
- ◆ For such simple description, one can use wire assignments
 - ◆ Hint: output is default wire-typed



Simulation

- ◆ There are two files in folder named “code”
 - ◆ HW2.v (homework)
 - ◆ HW2_tb.v (testbench)
- ◆ To run simulation, you should run source command in advance
 - ◆ `$ source 00_license.f` (use given file)



Simulation (cont.)

◆ Verilog simulation

- ◆ \$ source 01_run.f
- ◆ TA will run your code with following format of command in 01_run.f :

```
vcs ../00_TB/HW2_tb.v HW2.v -full64 -R -\  
debug_access+all +v2k +notimingcheck +define+I0
```

```
vcs ../00_TB/HW2_tb.v HW2.v -full64 -R -\  
debug_access+all +v2k +notimingcheck +define+I1
```

⋮

- ◆ The word in the block “I0” is the instruction set of test pattern, please change it from I0 to I7 to test your design.
- ◆ Make sure to pass every given testcase without any error messages.



Report (Snapshot, at Least One Table)

Register Name	Type	Width	Bus	MB	AR	AS	SR	SS	ST
alu_in_reg	Flip-flop	32	Y	N	Y	N	N	N	N
counter_reg	Flip-flop	5	Y	N	Y	N	N	N	N
shreg_reg	Flip-flop	64	Y	N	Y	N	N	N	N
state_reg	Flip-flop	2	Y	N	Y	N	N	N	N

- ◆ All sequential elements must be **flip-flops**
- ◆ **Make sure there is no latches in your design**
- ◆ Check by Design Compiler
- ◆ Command:
 - ◆ \$ dv -no_gui
 - ◆ design_vision> read_verilog HW2.v
- ◆ Exit:
 - ◆ design_vision> exit



Submission

- ◆ **Deadline: 23.59 pm on Nov. 20 (Mon.), 2023**
 - ◆ No late submissions are allowed
- ◆ Upload HW2_<student_id>_vk.zip to NTUCOOL
 - ◆ (k is the number of version, k = 1, 2, ...)
 - ◆ Use lower case for the letter in your student ID.
(Ex. HW2_b08901061_v1.zip)
 - ◆ Wrong file/folder format or additional files would result in **5-point** penalty each
 - ◆ HW2_<student_id>_vk.zip
 - HW2_<student_id>/
 - HW2_<student_id>/HW2.v
 - HW2_<student_id>/report.pdf
 - ◆ TA will only check the last version of your homework.



Grading Policy

- ◆ TA will check if your design is reasonable
 - ◆ Does NOT exist initial block and delay declaration
 - ◆ **Does NOT exist operators including “ * ” and “ / ”**
 - ◆ **Does NOT exist latches**
 - ◆ **Functionality would only be checked if the demands above are satisfied**
- ◆ Pass the patterns to get full score
 - ◆ Provided pattern: **80%** (I0 ~ I7)
 - **10%** for each set
 - **Don't implement your design directly based on the given testcases!**
 - ◆ Hidden pattern: **20%**
- ◆ Other rules:
 - ◆ Lose **5-point** for any wrong naming rule. Don't compress all homework folder.